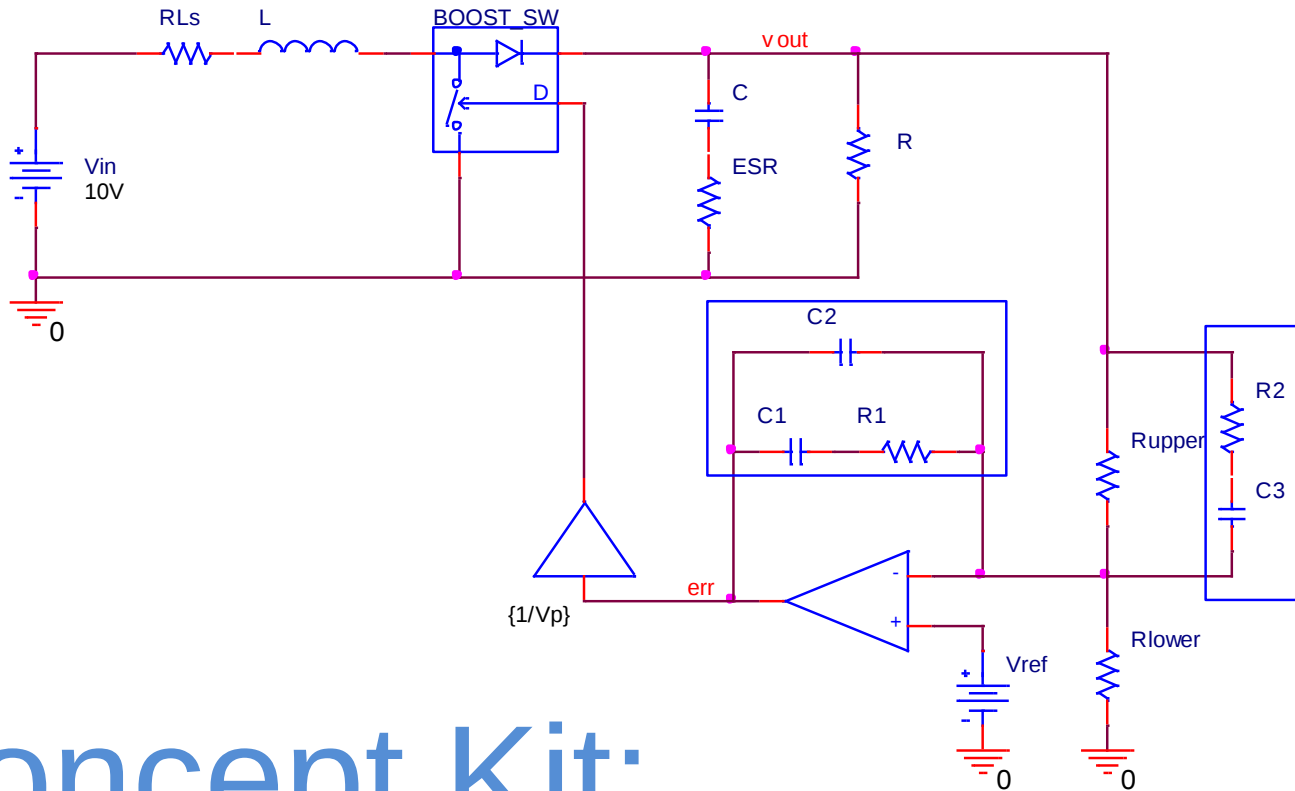




Concept Kit:


PWM Boost Converter Average Model

- The PWM Boost Converter Topology (Voltage Mode)
 - Averaged Boost Switch Model
- Boost Converter Design Workflow
 - Design Specification (Example)
 1. Setting PWM Controller's Parameters.
 2. Programming Output Voltage: R_{upper} , R_{lower}
 3. Inductor Selection: L , R_{LS}
 4. Capacitor Selection: C , ESR
 5. Stabilizing the Converter (Example)
- Load Transient Response Simulation (Example)


Appendix

- A. Boost Converter Calculator (Excel sheet)
- B. Feedback Loop Compensators
- C. Simulation Index

The PWM Boost Converter Topology

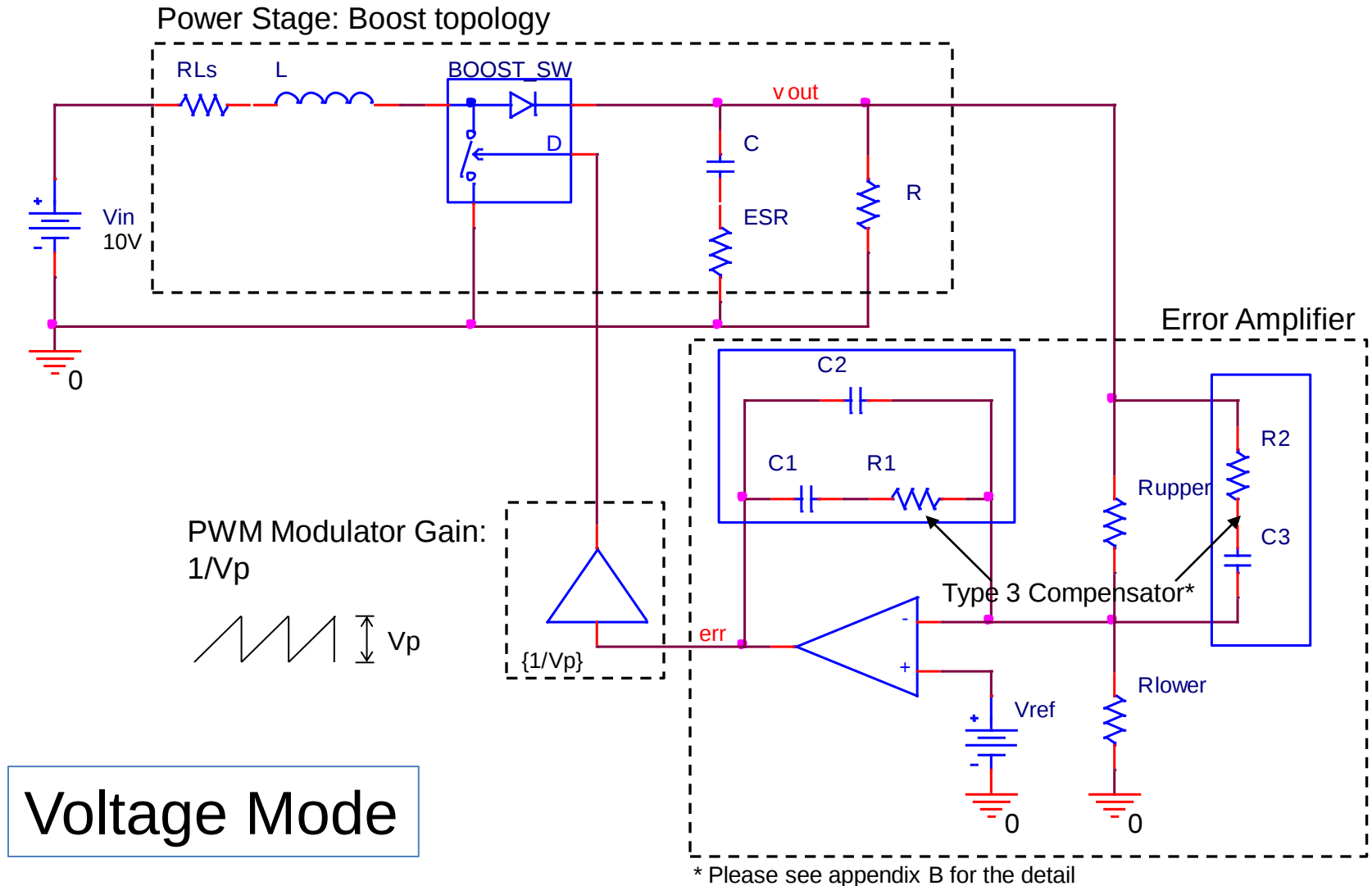

Averaged Boost Switch Model

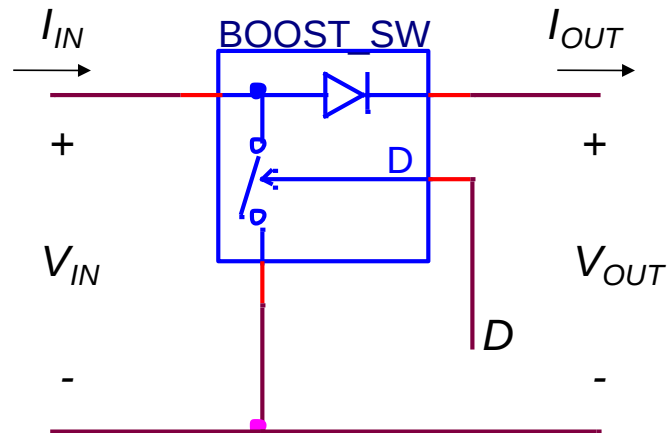


- The Averaged Boost Switch Model represents relation between input and output of the switch that is controlled by duty cycle – d (value between 0 and 1).


- Transfer function of the model is
$$V_{OUT} = \frac{V_{IN}}{(1-D)} \quad (1)$$

- The current flow into the switch is
$$I_{IN} = \frac{I_{OUT}}{(1-D)} \quad (2)$$

Boost Converter Design Workflow

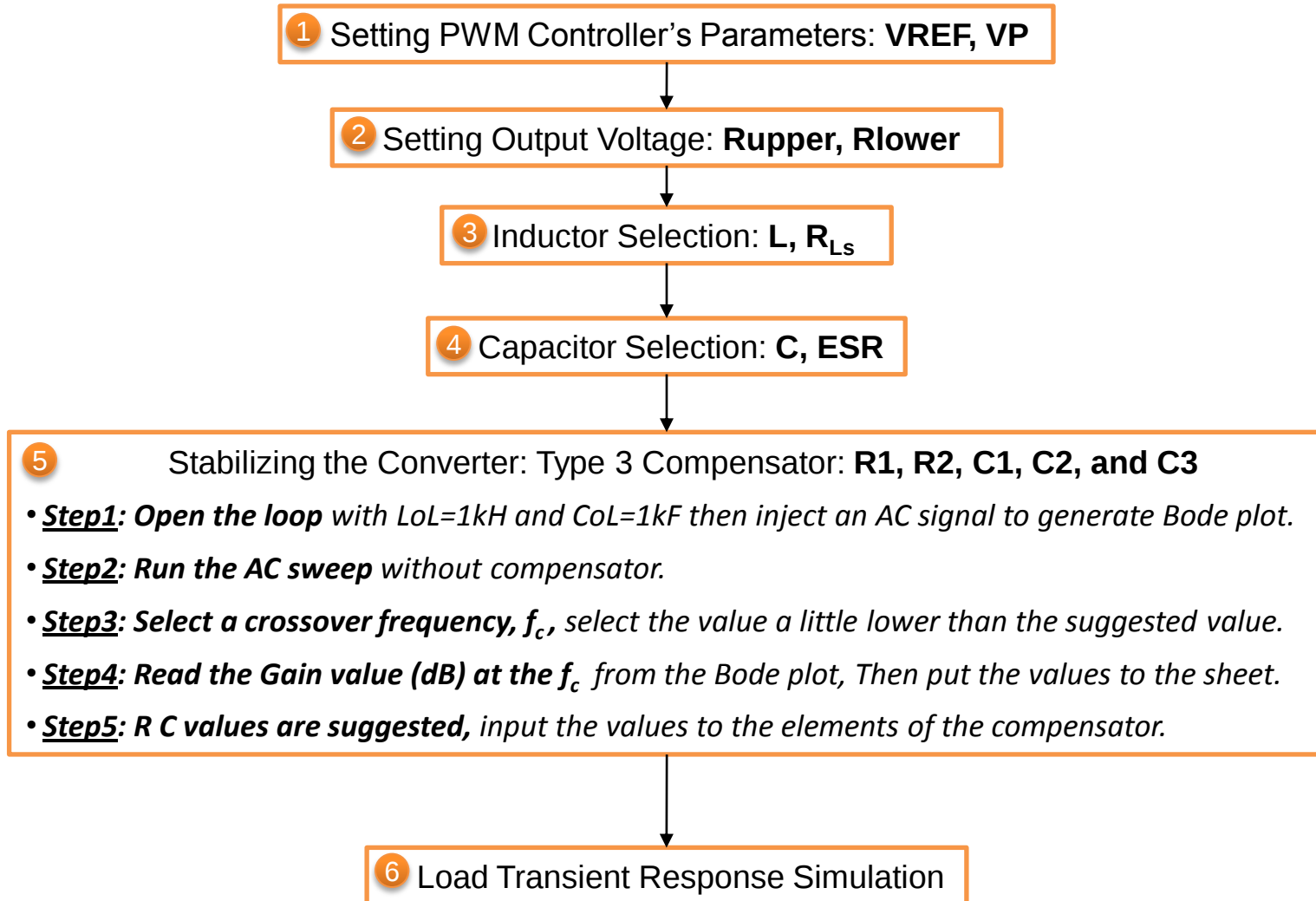

Buck Regulator Design Workflow

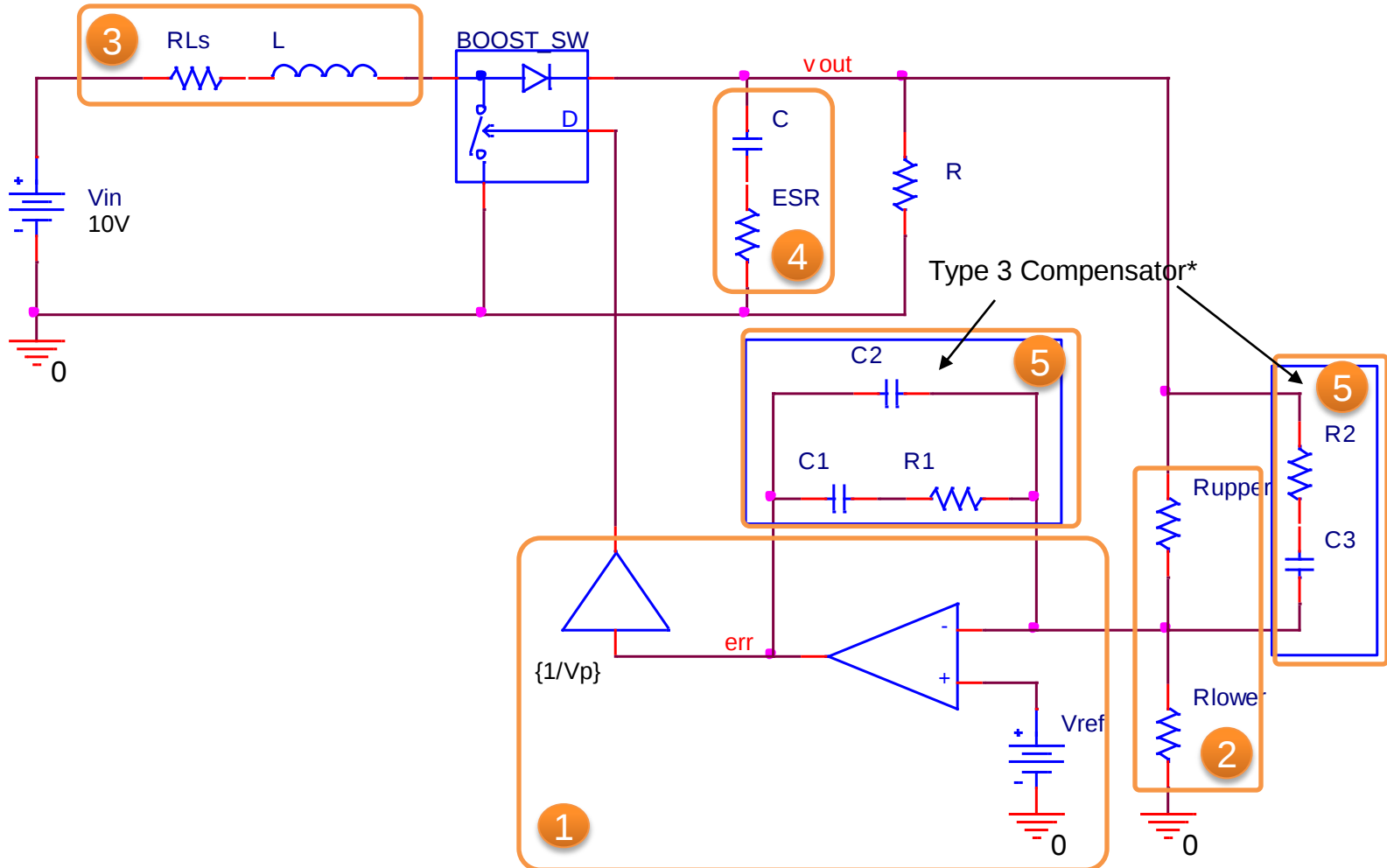

* Please see appendix B for the detail

Design Specification (Example)


A boost converter is designed to deliver 12V, 1.5A from a 3.3 V battery

Step-Up (Boost) Converter :


- $V_{in,max} = 3.63 \text{ (V)}$
 - $V_{in,min} = 2.97 \text{ (V)}$
 - $V_{out} = 12 \text{ (V)}$
 - $V_{out, ripple} = 180\text{mV}_{P-P} \text{ (1.2\%)}$
 - $I_{o,max} = 1.5 \text{ (A)}$
 - $I_{o,min} = 0.2 \text{ (A)}$
- $V_{in} = 3.3 \pm 10\%$

Control IC :

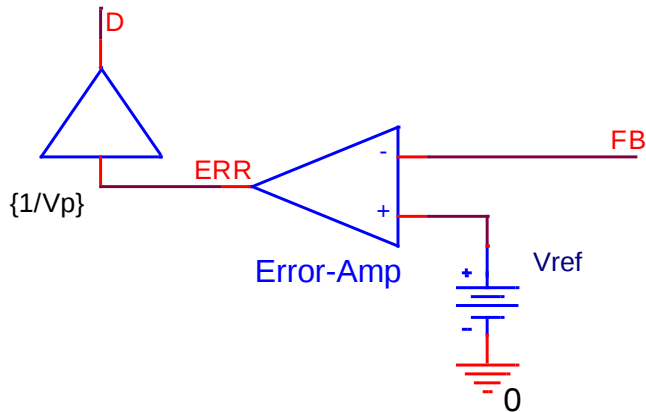- Part # TPS43000 (PWM Controller IC)
- Switching Frequency – $f_{osc} = 300 \text{ (kHz)}$



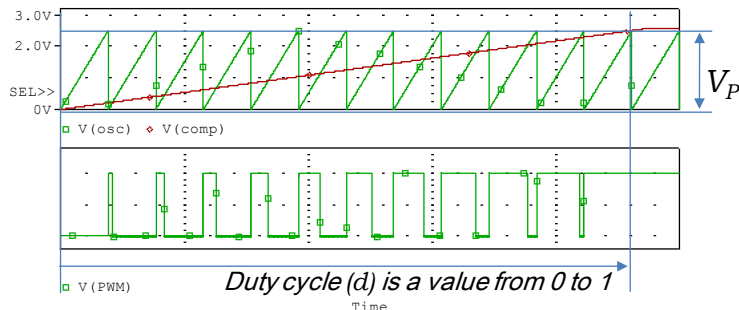The Error-Amp. is used to transfer the error voltage (between FB and V_{REF}) to be the duty cycle.



- **VREF**, feedback reference voltage, value is given by the datasheet
- **VP** = the sawtooth peak voltage.
 - If V_P does not provided, it could be calculated from:

$$VP = \Delta V_{FB} / \Delta d \quad (3)$$

$$\Delta V_{FB} = V_{FBH} - V_{FBL}$$

$$\Delta d = d_{MAX} - d_{MIN}$$

where

V_{FBH} is maximum FB voltage where $d = 0$

V_{FBL} is minimum FB voltage where $d = 1(100\%)$

d_{MAX} is maximum duty cycle, e.g. $d = 0(0\%)$

d_{MIN} is minimum duty cycle, e.g. $d = 1(100\%)$

- f_{osc} = Modulation frequency or switching frequency .

✖ If V_{FBH} and V_{FBL} are not provided, the default value, $VP=2$ could be used.

The VREF value is given by the datasheet

TPS43000 electrical characteristics

error amplifier

PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT
VREG, regulation voltage (COMP/FB pin)	$1.8\text{ V} < V_{IN} < 6\text{ V}$	784	800	816	mV
	$V_{IN} = 3.5\text{ V}$	788	800	812	
FB input current	$V_{FB} = 800\text{ mV}$	-150	-10	150	nA
Sourcing current (out of COMP)	$V_{FB} = (V_{REG} - 100\text{ mV})$, $V_{COMP} = 0\text{ V}$,		-2.0	-0.5	mA
Sinking current (into COMP)	$V_{FB} = (V_{REG} + 100\text{ mV})$, $V_{COMP} = 2\text{ V}$	0.5	1.2		mA
Maximum output voltage (COMP pin)	$V_{FB} = 0\text{ V}$, $I_{COMP} = -100\text{ }\mu\text{A}$	1.6	2.0		V
Minimum output voltage (COMP pin)	$V_{FB} = 2\text{ V}$, $I_{COMP} = +100\text{ }\mu\text{A}$		70	120	mV
Unity gain bandwidth	See Note 1		5		MHz

So we've got

$$V_{REF} = 0.8$$

The VP (sawtooth signal amplitude) can be calculated from the characteristics below.

TPS43000 electrical characteristics

PWM

PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT
BUCK threshold voltage	BUCK configured if $V_{BUCK} > 1\text{ V}$	0.4	0.7	1.0	V
BUCK pull-down current			0.5	1.0	μA
BUCK maximum duty cycle	$V_{FB} = 0\text{ V}$	100%			
BOOST maximum duty cycle	BUCK grounded, $V_{FB} = 0\text{ V}$	70%	90%		
Minimum duty cycle	$V_{FB} = 2\text{ V}$			0%	
CCM threshold voltage	Continuous conduction allowed if $V_{CCM} > 1\text{ V}$	0.4	0.7	1.0	V
CCM pull-down current			0.5	1.0	μA
BUCK rectifier zero current threshold voltage	Measured from SWP to GND	-28	-12	0	mV
BOOST rectifier zero current threshold voltage	Measured from SWP to VOUT, BUCK grounded	0	14	32	mV
Delay to termination of P-channel gate drive time	Measured at PDRV, BUCK grounded		200	300	ns

from eq. (3)

$$VP = \Delta V_{FB} / \Delta d$$

- from the datasheet , $\Delta V_{FB} = (2-0) = 2\text{ V}$, and $\Delta d = (0.9-0) = 0.9$

$$\begin{aligned}
 VP &= 2 / 0.9 \\
 &= 2.2
 \end{aligned}$$

2 Programming Output Voltage: Rupper, Rlower

- Use the following formula to select the resistor values.

$$V_{out} = V_{ref} \left(1 + \frac{R_{upper}}{R_{lower}} \right) \quad (4)$$

Example

Given: $V_{out} = 12V$


$V_{ref} = 0.8$

$R_{lower} = 10k$

then:

$$R_{upper} = \frac{(V_{OUT} - V_{REF}) \times R_{lower}}{V_{REF}}$$

$$R_{upper} = 140k$$

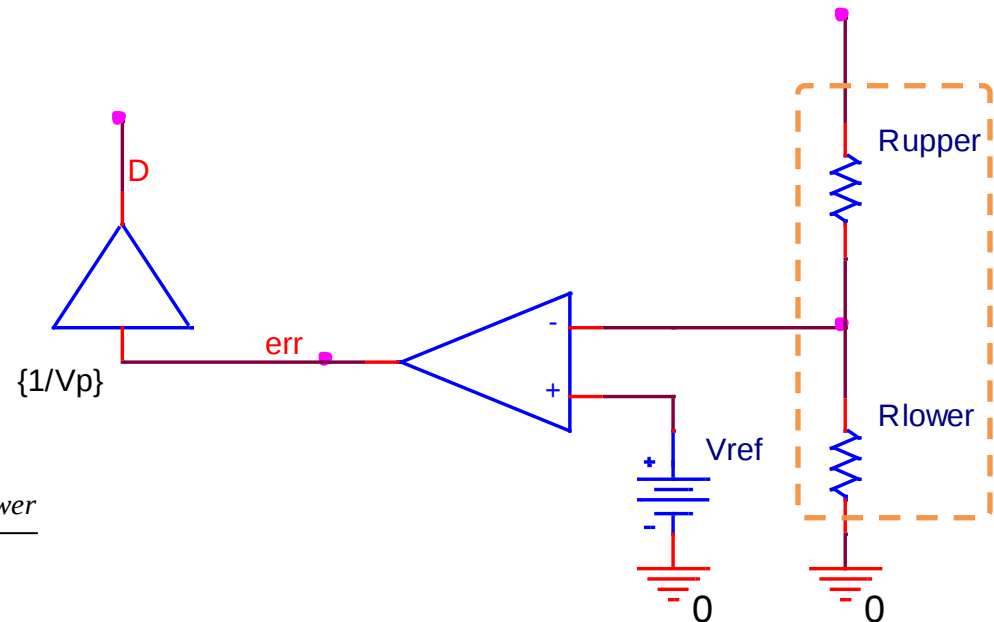


2 Programming Output Voltage: Rupper, Rlower


- This calculation could be completed by using **the Boost Converter Calculator (Excel sheet)**.
- After input all the boost converter specs and the R_{lower} value then R_{upper} is automatically calculated

Boost Converter Calculator (Excel sheet)


The following specs are needed to calculate the power stage:

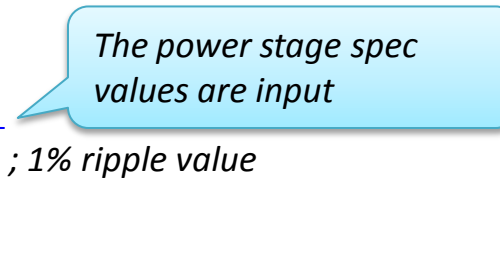Spec:	$V_{in,max}$	3.63 V	
	$V_{in,min}$	2.97 V	
	V_{out}	12 V	
	$V_{out,ripple}$	0.18 V	
	$I_{o,max}$	1.5 A	
	$I_{o,min}$	0.2 A	

The following specs are needed to calculate the controller stage:

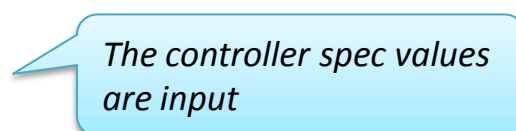❶	V_{REF}	0.8 V	
	V_p	2.2 V	
	f_{osc}	300 kHz	

❷	R_{lower}	10 k Ω	
	R_{upper}	140 k Ω	

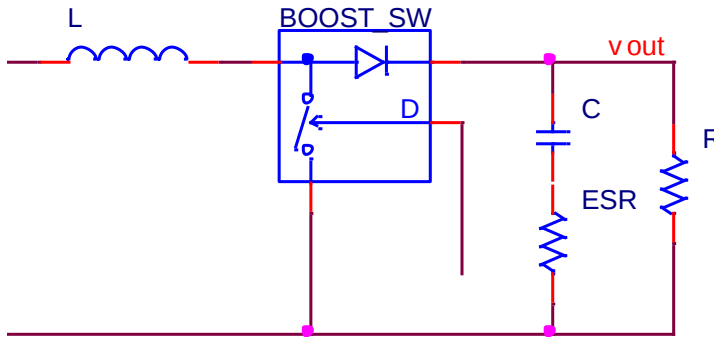

Inductor Value

- The output inductor value is selected to set the converter to work in CCM (Continuous Current Mode) for all load current conditions.
- Calculated by

$$L_{CCM} \geq \frac{D_{\min} \cdot (1 - D_{\min})^2 \cdot V_{OUT}}{2 \cdot f_{osc} \cdot I_{O, \min}} \quad (5)$$


- with

$$\Delta I_L = \frac{V_{in, \min} \cdot D_{\max}}{L \cdot f_{osc}} \quad (6)$$

Where

- L_{CCM} is the inductor that make the converter to work in CCM.
- $D_{\max}$ is the maximum duty cycle; $D_{\max} = 1 - V_{in, \min} / V_{OUT}$
- R_{LS} is load resistance at the minimum output current ($I_{O, \min}$)
- f_{osc} is switching frequency
- ΔI_L is inductor ripple current

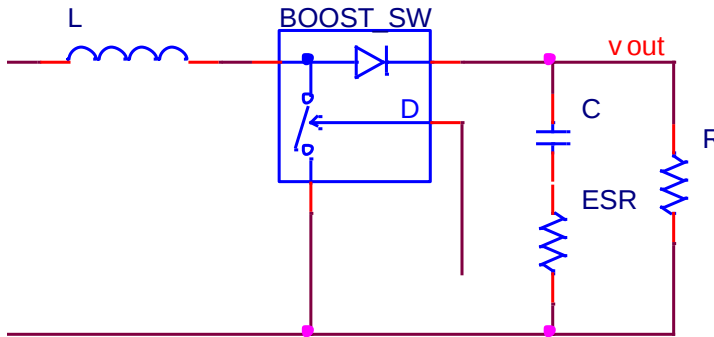3 Inductor Selection: L, R_{LS} (Example)



Inductor Value

from eq. (5)

$$L_{CCM} \geq \frac{D_{\min} \cdot (1 - D_{\min})^2 \cdot V_{OUT}}{2 \cdot f_{osc} \cdot I_{O, \min}}$$

Given:

- $V_{in, \max} = 3.63V$ (3.3V+10%), $V_{out} = 12V$, $I_{O, \min} = 0.2A$
- $D_{\min} = 1 - V_{in, \max} / V_{out} = 0.7$
- $f_{osc} = 300kHz$

Then:

- $L_{CCM} \geq 64$ (uH),
- $L = 68$ (uH) is selected

3 Inductor Selection: L , R_{LS} (Example)

- This calculation could be completed by using **the Boost Converter Calculator (Excel sheet)**.
- After input all the known parameters, this sheet will suggest the inductor L value, using eq. (5)

$$D_{max} \quad 0.75$$

$$D_{min} \quad 0.70$$

$$; = 1 - V_{in,min} / V_{out}$$

$$; = 1 - V_{in,max} / V_{out}$$

D_{max} and D_{min} are auto-calculated

$$\textcircled{3} \quad L > \quad 6.4 \text{ uH}$$

$$L = \quad 6.8 \text{ uH}$$

$$R_{LS} \quad 10 \text{ m}\Omega$$

$$\Delta I_L \quad 1.10\text{E}+00 \text{ A}$$


; suggested inductor L value (from eq.5)

; the selected inductor L value

; the selected inductor, series resistance value

; calculated inductor ripple current (from eq.6)

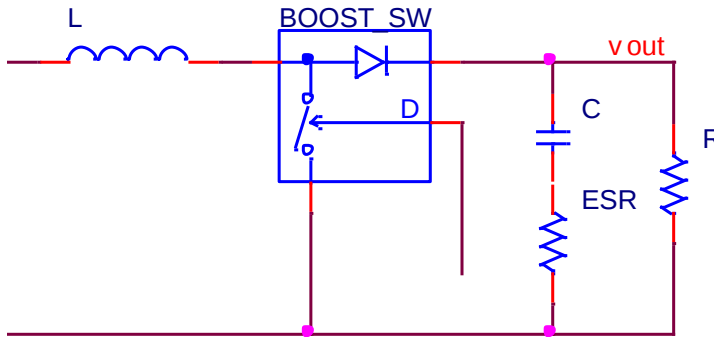The excel sheet suggests an inductor value, by using eq. (5). Then input your inductor L value ($>$ suggested value), and R_{LS} value of the inductor for further calculation.



Capacitor Value

- The minimum allowable output capacitor value should be determined by


$$C \geq \frac{D_{\max} \cdot I_{o, \max}}{V_{out, ripple} \cdot f_{OSC}} \quad (7)$$

- In addition, the capacitor must be able to handle the current more than

$$I_{C, Rated} \approx \frac{\Delta I_L}{2} \quad (8)$$

- Where ΔI_L is calculated by eq. (6)
- The ESR of the output capacitor adds some more ripple, so it should be limited by following equation:
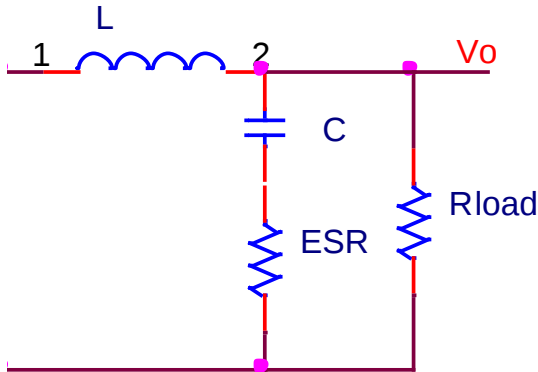
$$ESR \leq \frac{V_{out, ripple}}{I_C} \quad (9)$$



Capacitor Value

From eq. (7)

$$C \geq \frac{D_{\max} \cdot I_{o, \max}}{V_{out, \text{Ripple}} \cdot f_{OSC}}$$

and eq. (8) and eq. (9)

$$I_C \approx \frac{\Delta I_L}{2} \quad ESR \leq \frac{V_{out, \text{ripple}}}{I_C}$$

Given:

- $D_{\max} = 0.75$ V
- $I_{o, \max} = 1.5$ A
- $V_{out, \text{ripple}} = 0.18$ V

Then:

- $C \geq 20.9$ (μF)

In addition:

- $I_{C, \text{Rated}} \approx 550\text{mA}$
- $ESR \leq 27\text{m}\Omega$

4 Capacitor Selection: C, ESR (Example)

- This calculation could be completed by using **the Boost Converter Calculator (Excel sheet)**.
- After input all the known parameters, this sheet will suggest the capacitor C and ESR value, using eq. (7) and eq. (9).

④	$C \geq$	20.9 μF	; eq. (7) suggested value
	C	1410 μF	; the selected Capacitor C value
	$ESR <$	0.027 Ω	; eq. (9) suggested value
	$ESR =$	0.027 Ω	; the selected capacitor ESR value
	$I_{C,Rated} \approx$	0.55 A	; Rated ripple current


The excel sheet suggests an capacitor value, by using eq. (7) and ESR value by using eq. (9). Then input your capacitor C Value and the capacitor's ESR value for further calculation. The capacitor's rated current should be more than the suggested value I_C

- A SMD type electrolytic capacitor from NIPPON CHEMI-CON, part no. EMZJ160ADA471MHA0G is selected with the following characteristics.

EMZJ160ADA471MHA0G

$C =$	470 μF
V_{dc}	16 V
$ESR =$	0.08 Ω
<i>Rated Ripple Current</i>	0.85 A_{rms}

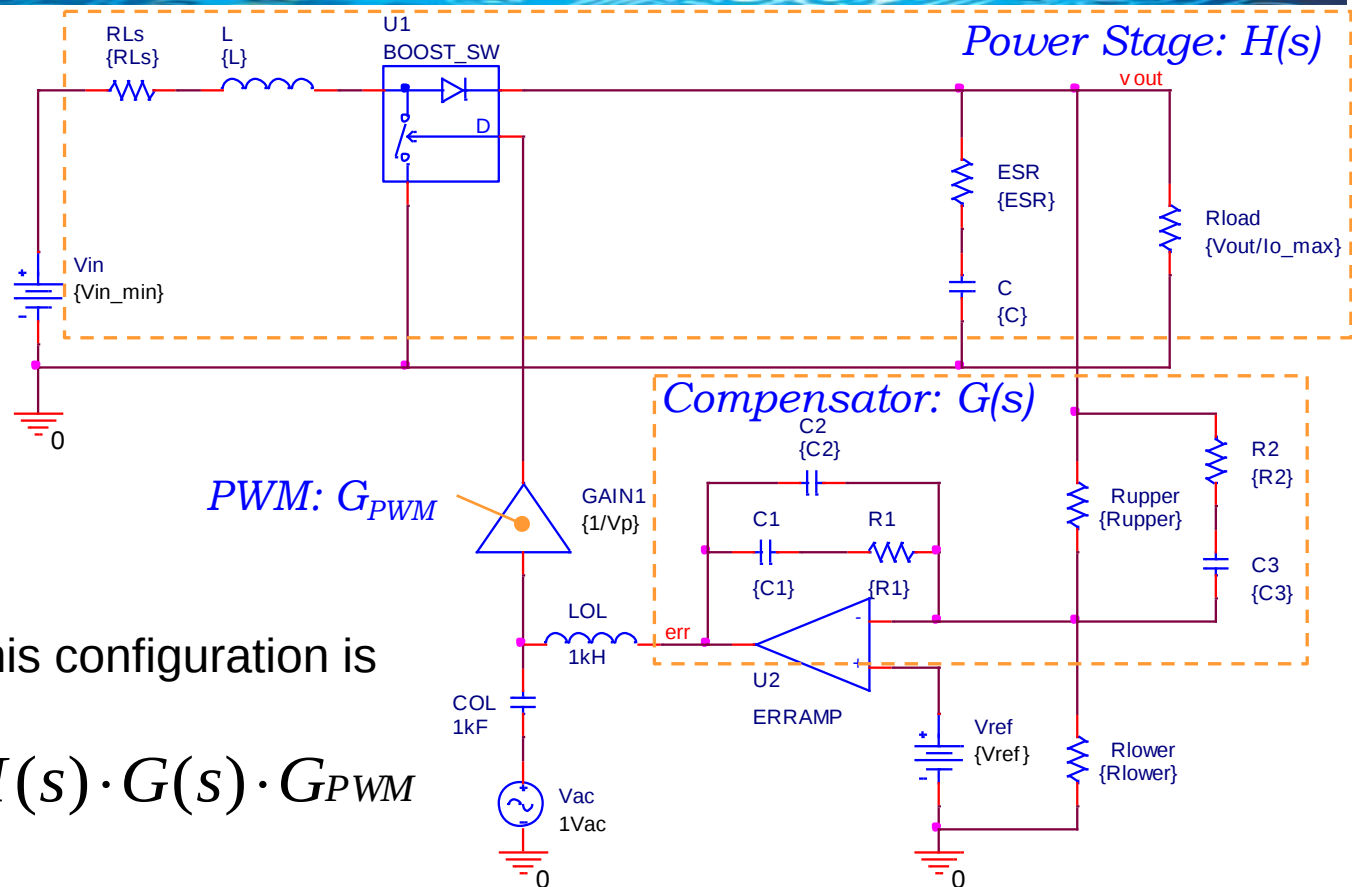- The suggested ESR should be less than 27 m Ω , three of these part will be put in parallel to meet the converter specs.
- So we select the capacitor C value = $470\mu F \times 3 = 1410 \mu F$, with $ESR = 0.08\Omega / 3 = 0.027\Omega$



- Loop gain for this configuration is

$$T(s) = H(s) \cdot G(s) \cdot G_{PWM}$$

- The purpose of the compensator $G(s)$ is to tailor the converter loop gain (frequency response) to make it stable when operated in closed-loop conditions.

5 Stabilizing the Converter (Example)

Converter parameters

PARAMETERS:

$V_{in_min} = 2.97$

$V_{out} = 12V$

$I_{o_max} = 1.5A$

$V_{ref} = 0.8$

$V_p = 2.2$

$R_{lower} = 10k$


$R_{upper} = 140k$

$L = 6.8u$

$RLS = 10m$

$C = 1410u$

$ESR = 27m$

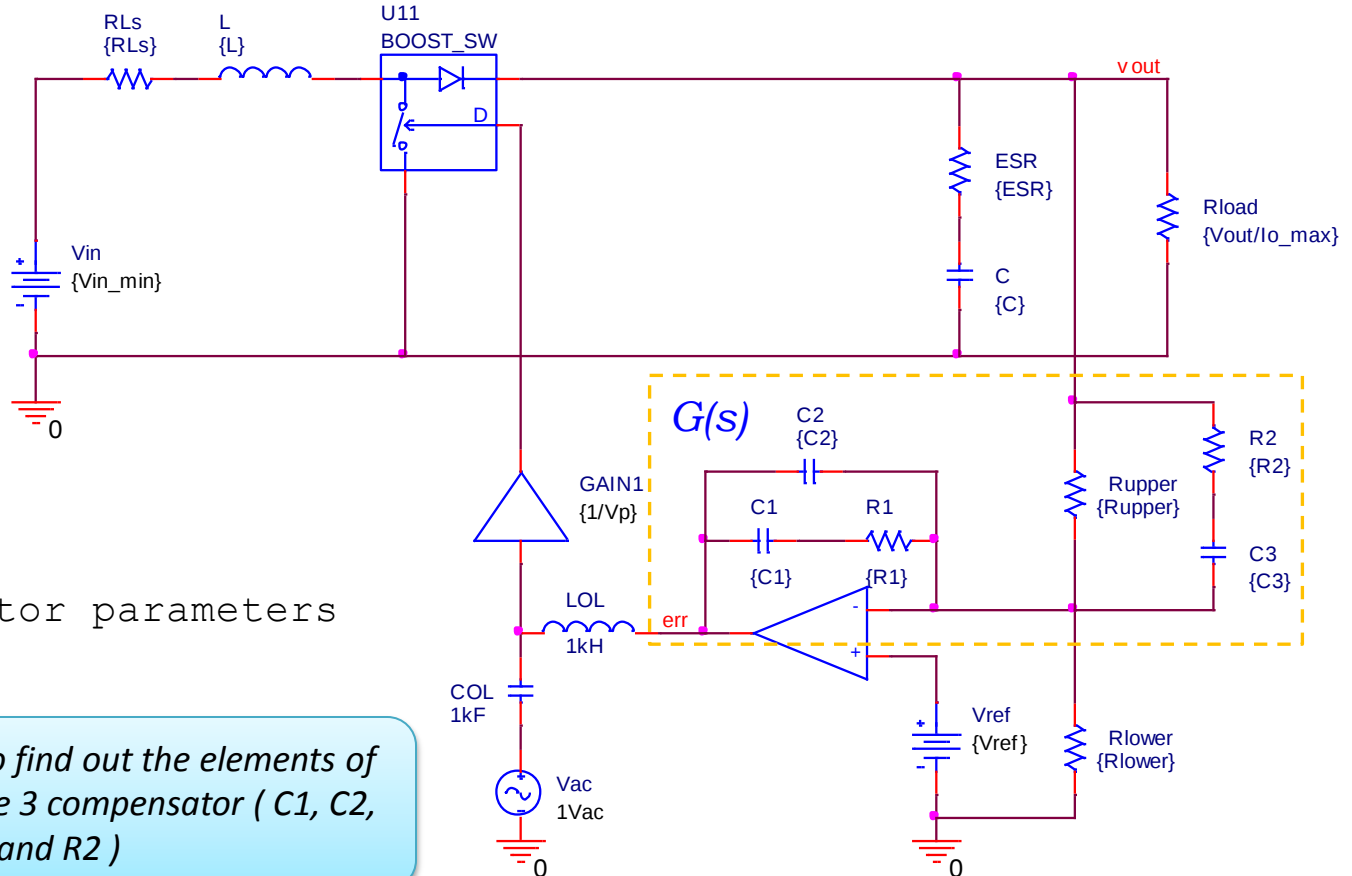

Type 3 compensator parameters

PARAMETERS:

$C1 = ?$

$C2 = ?$

$C3 = ?$

$R1 = ?$

$R2 = ?$

Task: to find out the elements of the Type 3 compensator ($C1$, $C2$, $C3$, $R1$, and $R2$)

Frequency Response without Compensator.

Converter parameters

PARAMETERS:

Vin_min = 2.97

Vout = 12V

Io_max = 1.5A

Vref = 0.8

Vp = 2.2

Rlower = 10k


Rupper = 140k

L = 6.8u

RLS = 10m

C = 1410u

ESR = 27m

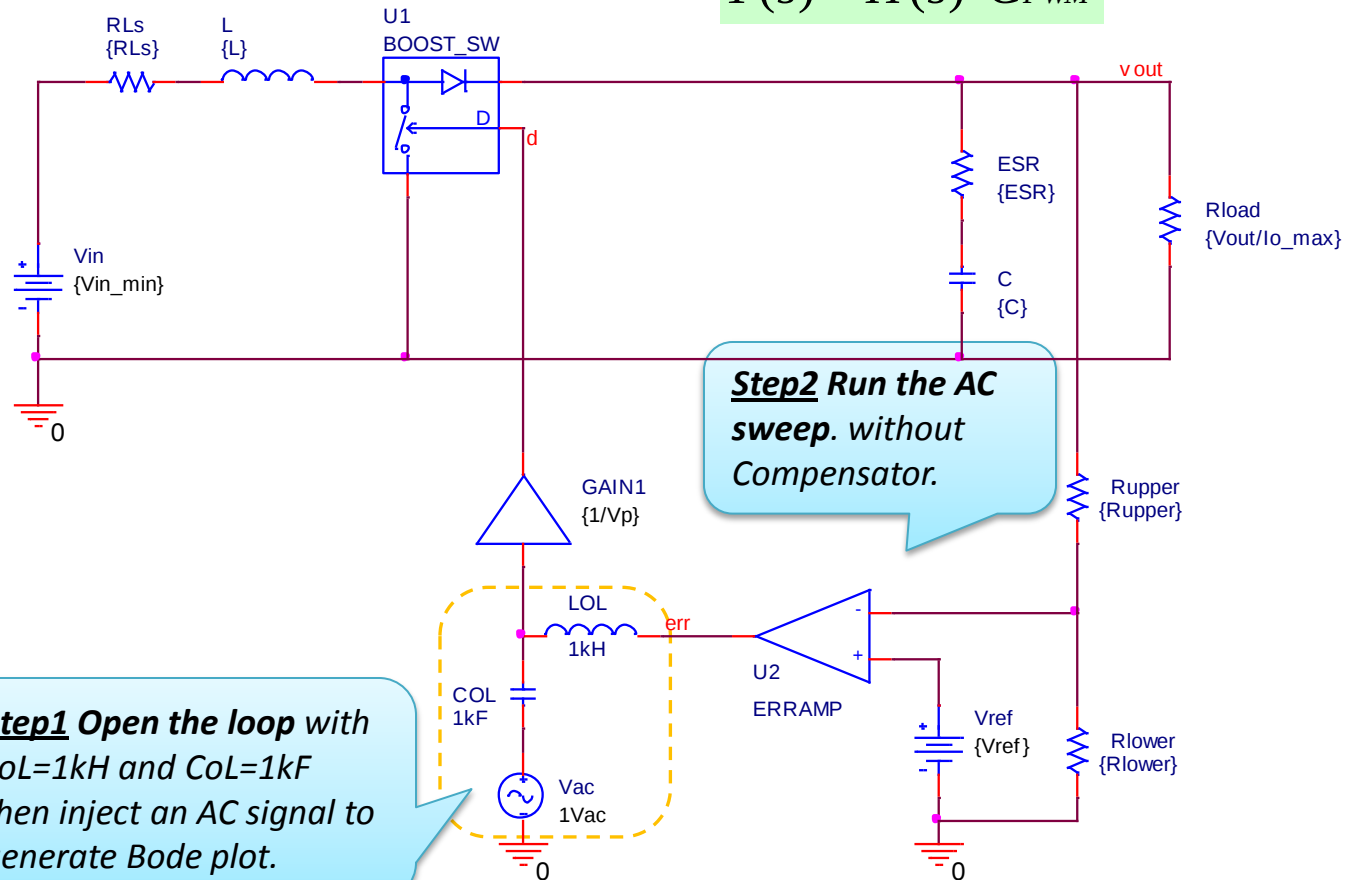

$$T(s) = H(s) \cdot G_{PWM}$$

Step2 Run the AC sweep. without Compensator.

Step1 Open the loop with $LoL=1kH$ and $CoL=1kF$ then inject an AC signal to generate Bode plot.

※ $C1=1kF$ is AC shorted, and $C2 1fF$ is AC opened (or Error-Amp without compensator).

5 Stabilizing the Converter (Example)

- This calculation could be completed by using **the Boost Converter Calculator (Excel sheet)**.
- After input all the known parameters, this sheet will suggest the crossover frequency f_c value, and the maximum input voltage $V_{in,max}$.

Step3 Select a crossover frequency- f_c
 the maximum f_c is automatically calculated from the boost converter spec and condition. Select the value a little lower than the suggested value.

Type 3 Compensator Calculator


$$R_{load,min} \quad 8 \, \Omega \quad ; = V_{out}/I_{o,min}$$

$$f_c < \quad 3440.91 \, \text{Hz} \quad ; f_c < 0.3 \text{ times RHPZ, } f_{z2}$$

$$f_c = \quad 3000 \, \text{Hz} \quad ; \text{ select the value of } f_c$$

$$V_{in,max} < \quad 7.38 \, \text{V} \quad ; V_{in,max} \text{ suggested value}$$

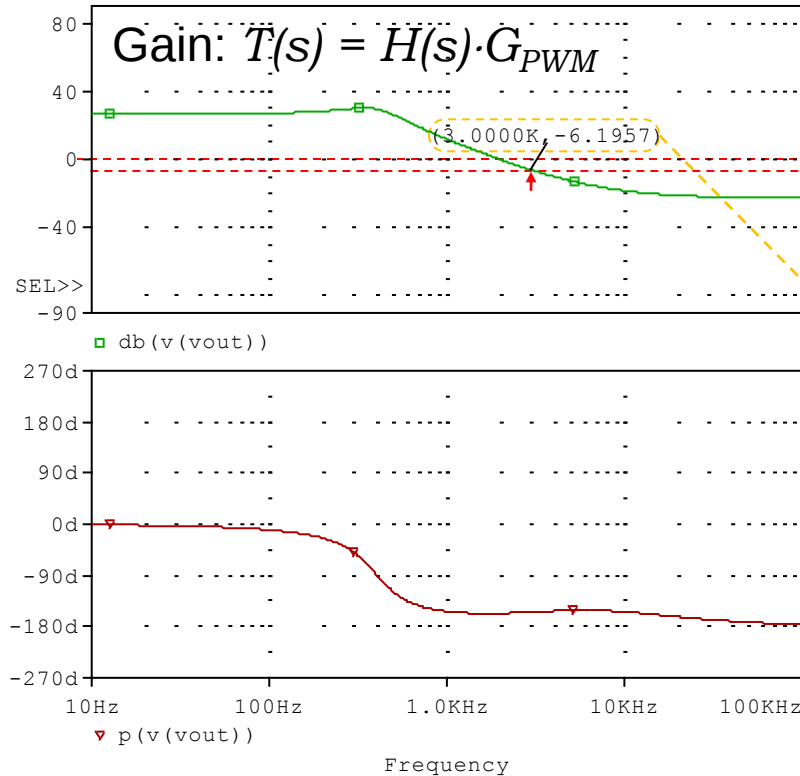The $V_{in,max}$ suggested value shows the maximum input voltage that the converter could be used.



Frequency Response **without** Compensator.

Step4 Read the Gain value (dB) at the f_c from the Bode plot, Then put the values to the sheet.

Compensator:

$G @ f_c$ -6.2 dB ; read from the simulation result
 G 2.042 ; compensation gain

Tip: To bring cursor to the $f_c = 3kHz$ type “**sfxv(3k)**” in Search Command.



Cursor Search

5 Stabilizing the Converter (Example)

- This calculation could be completed by using **the Boost Converter Calculator (Excel sheet)**.
- After input all the known parameters, this sheet will suggest the **C1, C2, C3, R1, and R2** values.

Compensator:

$f_{z,double}$ 402Hz ; double zero use to compensate the LC filter peak (resonant)
 f_{p1} 4181Hz ; a first pole use to compensate an ESR effect
 f_{p2} 11470Hz ; a second pole use to compensate RHP zero

a 8.39E+13

c 3.72E+15

Compensator components:

Step5 R C values are suggested, input the values to the elements of compensator.

5	C1	8.259 nF
	C2	0.795 nF
	C3	2.826 nF
	R1	47.9 kΩ
	R2	4.9 kΩ

※ Please note that the capacitor C value (from 4) needs to be big enough to make $f_{p2} > f_{p1}$ for the best result in calculation.

Frequency Response *with* Compensator.

Converter parameters

PARAMETERS:

$V_{in_min} = 2.97$

$V_{out} = 12V$

$I_{o_max} = 1.5A$

$V_{ref} = 0.8$

$V_p = 2.2$

$R_{lower} = 10k$


$R_{upper} = 140k$

$L = 6.8u$

$RLS = 10m$

$C = 1410u$

$ESR = 27m$

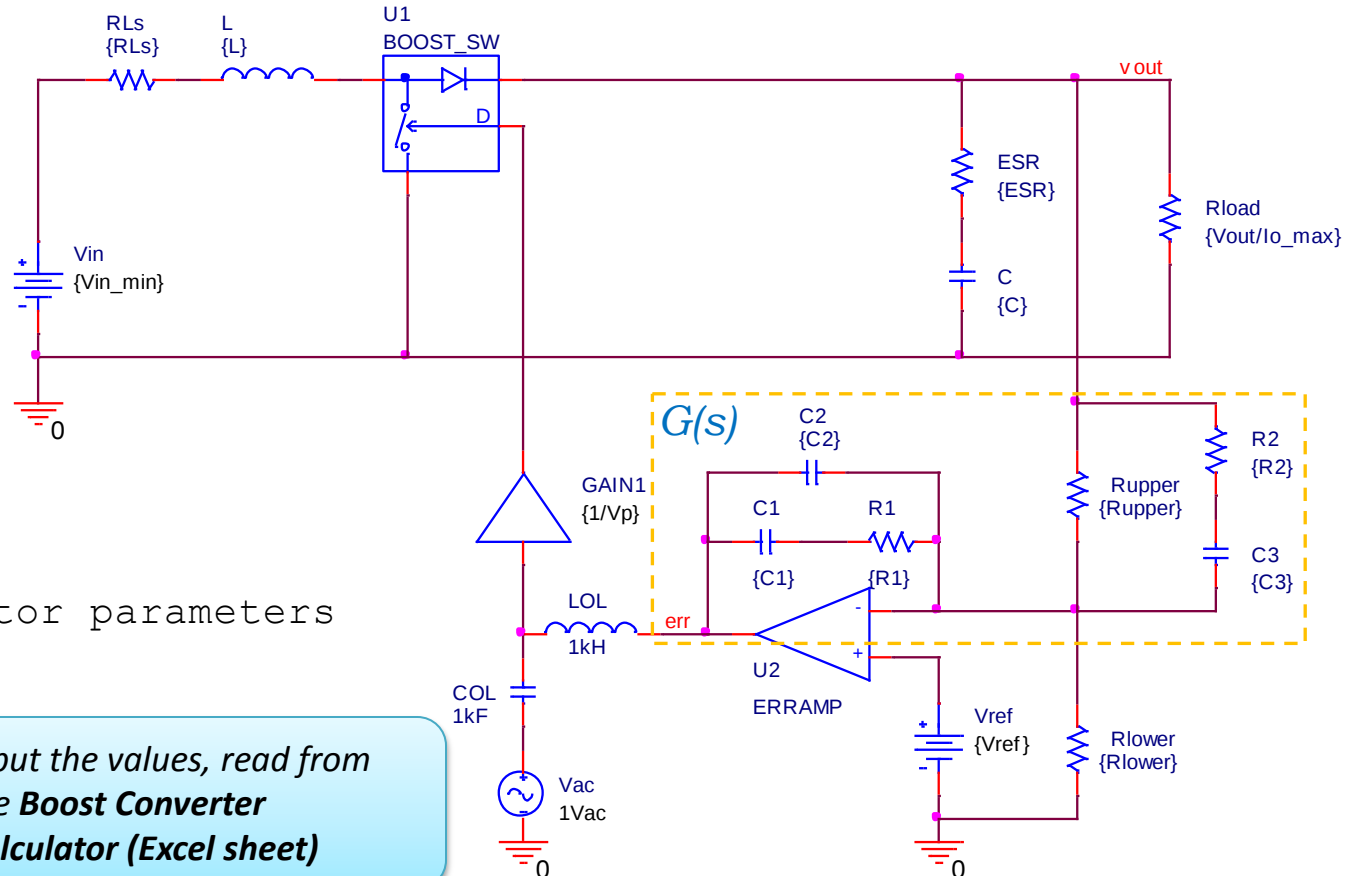

Type 3 compensator parameters

PARAMETERS:

$C1 = 8.259n$

$C2 = 795p$


$C3 = 2.826n$

$R1 = 47.9k$

$R2 = 4.9k$

*Input the values, read from
the **Boost Converter
Calculator (Excel sheet)***

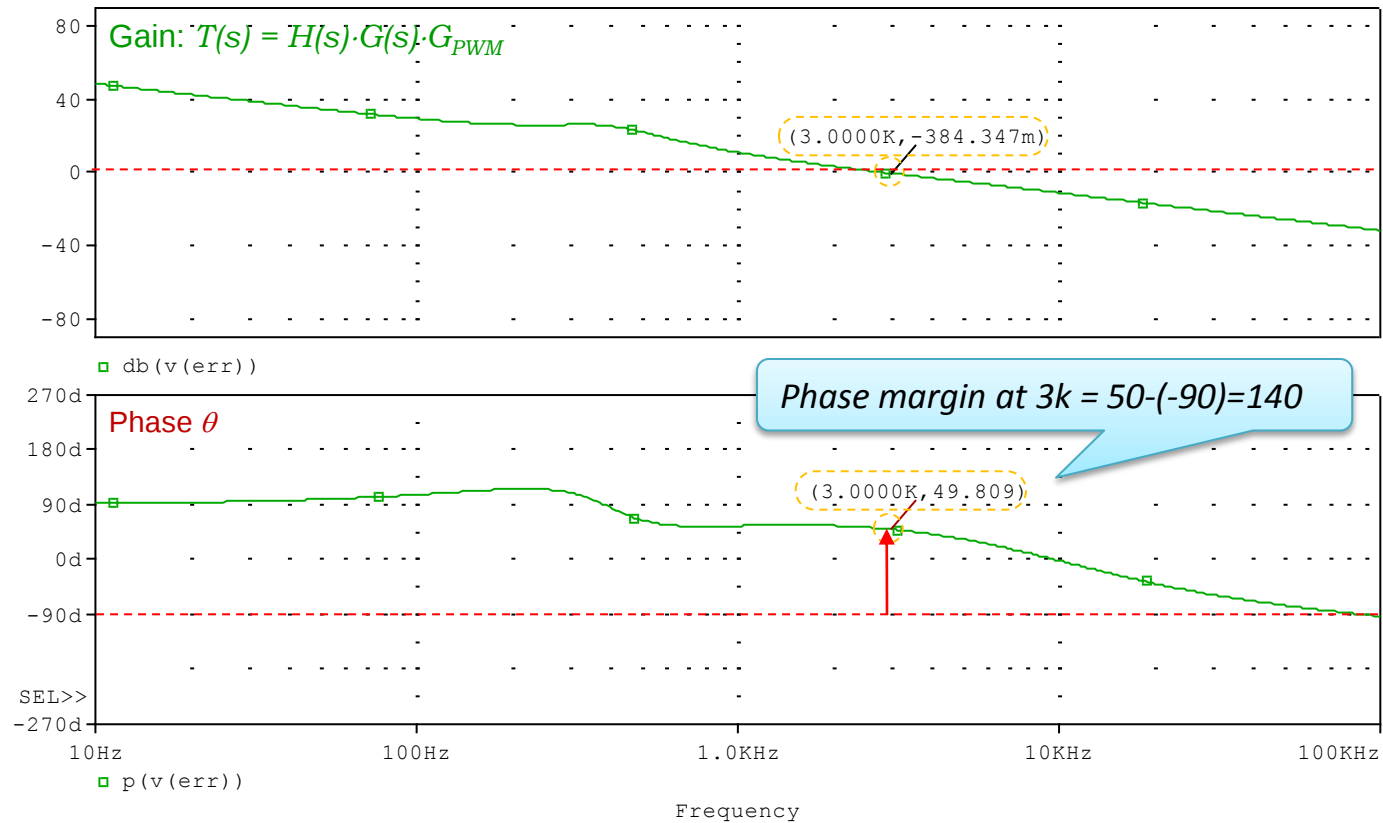Gain and Phase responses after stabilizing



- Phase margin = 140 at 3kHz.

Load Transient Response Simulation (Example)

The converter, that have been stabilized, are connected with step-load to perform load transient response simulation.

Converter parameters


PARAMETERS:

Vin_min = 2.97
Vout = 12V
Io_max = 1.5A
Vref = 0.8
Vp = 2.2
Rlower = 10k
Rupper = 140k
L = 6.8u
RLS = 10m
C = 1410u
ESR = 27m

Type 3 compensator parameters


PARAMETERS:

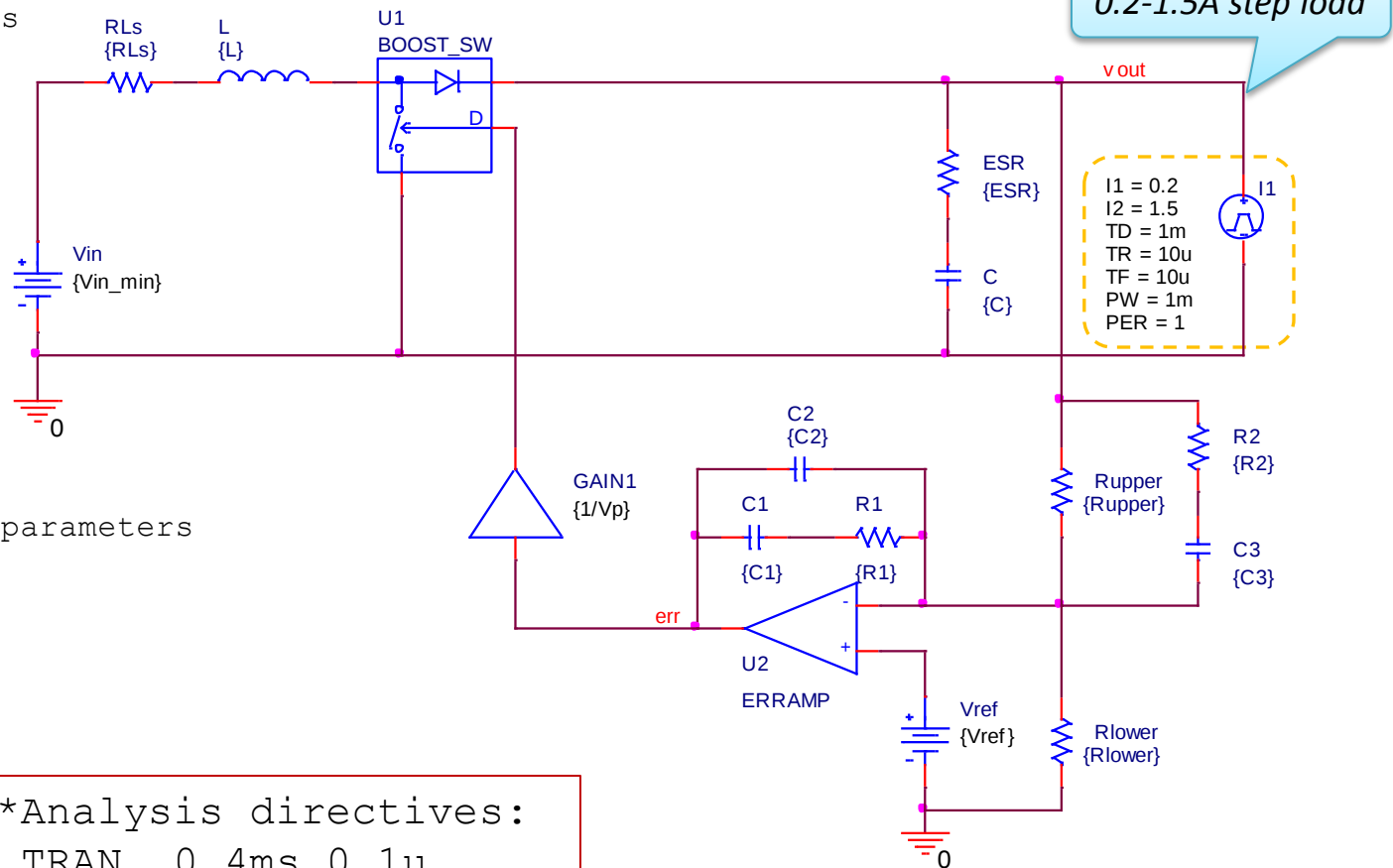C1 = 8.259n
C2 = 795p
C3 = 2.826n
R1 = 47.9k
R2 = 4.9k



*Analysis directives:
.TRAN 0 4ms 0 1u

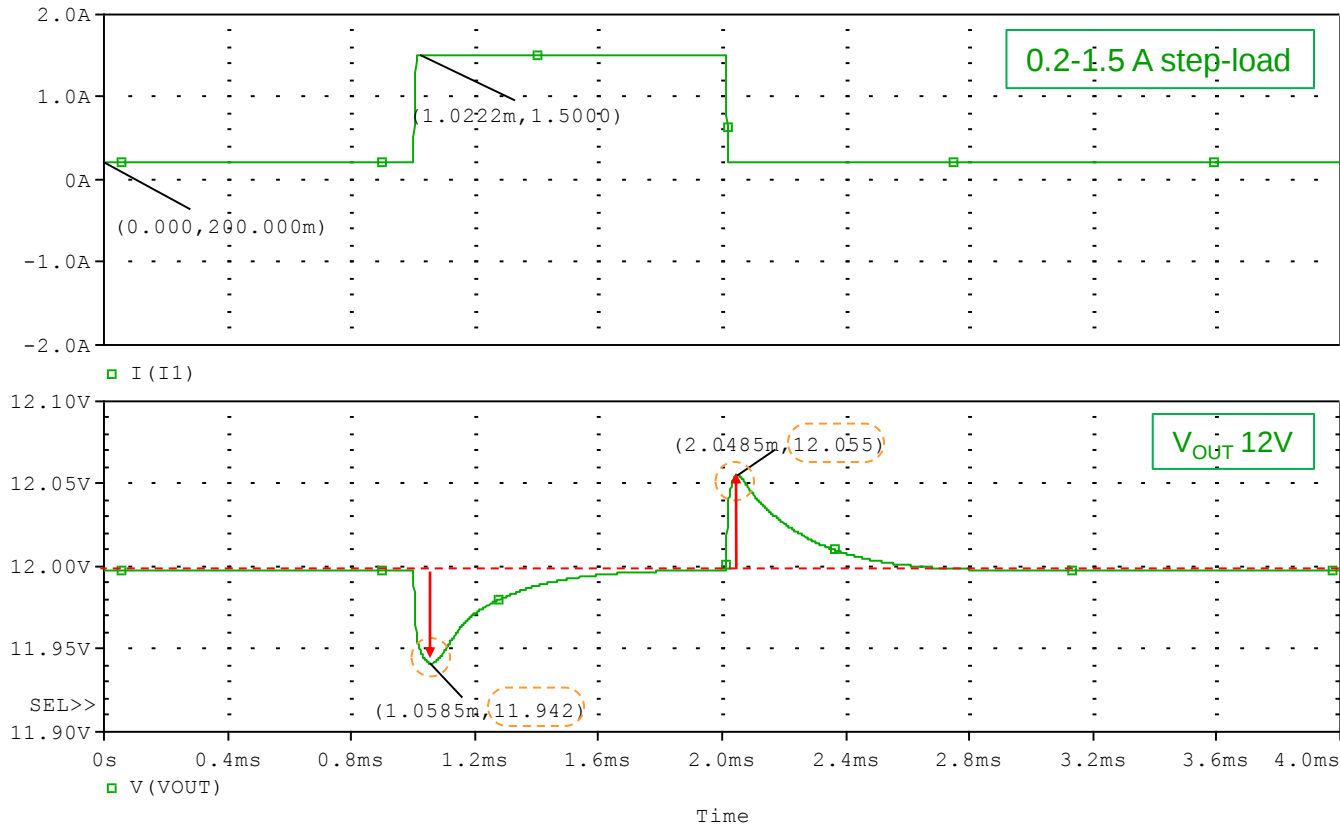Step-load transient responses after stabilizing



- The simulation result shows undershoot and overshoot voltages caused by step-load, that are below 120mV or less than 1% of the output.

A. Boost Converter Calculator (Excel sheet) 1/3

Boost Converter Calculator (Excel sheet)

The following specs are needed to calculate the power stage:

Spec: $V_{in,max}$	3.63 V	; +10% of 3.3V
$V_{in,min}$	2.97 V	; -10% of 3.3V
V_{out}	12 V	
$V_{out,ripple}$	0.18 V	; 1.5% ripple value
$I_{o,max}$	1.5 A	
$I_{o,min}$	0.2 A	

A. Boost Converter Calculator (Excel sheet) 2/3

The following specs are needed to calculate the controller stage:

❶	V_{REF}	0.8 V
	V_p	2.2 V
	f_{OSC}	300 kHz

❷	R_{lower}	10 k Ω
	R_{upper}	140 k Ω

	D_{max}	0.75	; $= 1 - V_{in,min}/V_{out}$
	D_{min}	0.70	; $= 1 - V_{in,max}/V_{out}$

❸	$L >$	6.4 μ H	; suggested inductor L value
	$L =$	6.8 μ H	; the selected inductor L value
	$R_{Ls} =$	10.0 m Ω	; the selected inductor, series resistance value
	ΔI_L	1.10E+00 A	; calculated inductor ripple current

❹	$C \geq$	20.9 μ F	; eq. (7) suggested value
	C	1410 μ F	; the selected capacitor C value
	$ESR \leq$	0.027 Ω	; eq. (9) suggested value
	$ESR =$	0.027 Ω	; the selected capacitor ESR value
	$I_{C,Rated} =$	5.48E-01	; Rated ripple current

A. Boost Converter Calculator (Excel sheet) 3/3

Type 3 Compensator Calculator

$R_{load,min}$	<u>8Ω</u>	; $= V_{out}/I_{o,min}$
$f_c <$	<u>3440.91Hz</u>	; $f_c < 0.3$ times RHP zero
$f_c =$	<u>3000Hz</u>	; the selected f_c value
$V_{in,max} <$	<u>7.38V</u>	; $V_{in,max}$ suggested value

Compensator:


$G @ f_c$	<u>-6.2dB</u>	; read from the simulation result
G	<u>2.042</u>	; compensation gain
$f_{z,double}$	<u>402Hz</u>	; double zero use to compensate the LC filter peak (resonant)
f_{p1}	<u>4181Hz</u>	; a first pole use to compensate an ESR effect
f_{p2}	<u>11470Hz</u>	; a second pole use to compensate RHP zero
a	<u>8.39E+13</u>	
c	<u>3.72E+15</u>	

Compensator components:


5

C1	8.259nF
C2	0.795nF
C3	2.826nF
R1	47.9kΩ
R2	4.9kΩ


B. Feedback Loop Compensator

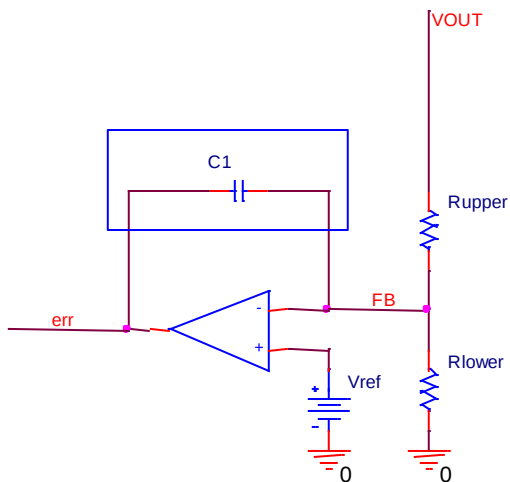

Type1 Compensator

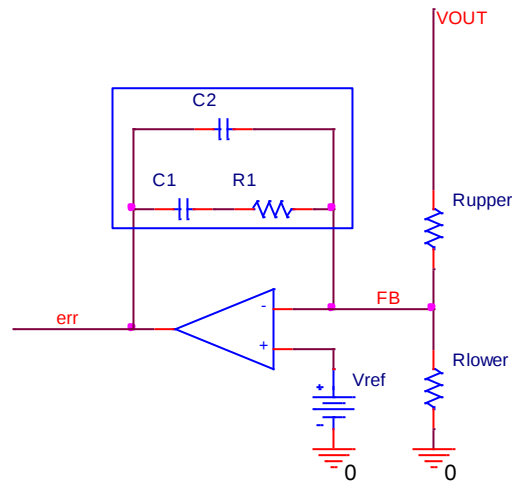

Type2 Compensator

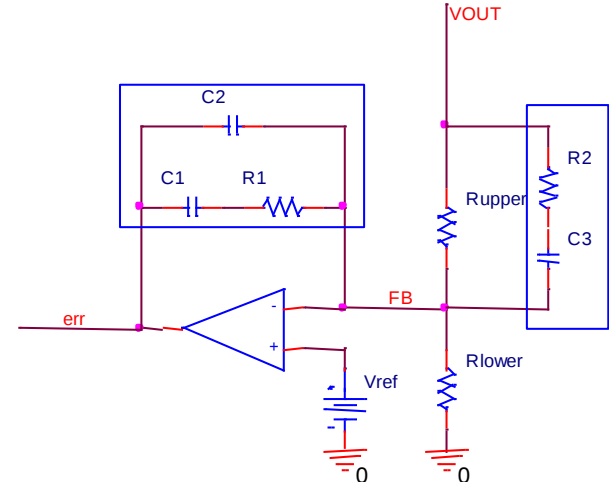

Type3 Compensator

- Because the boost converter is a 2nd order system, so the Type3 compensator are needed

C. Simulation Index

Simulations

Folder name

- | | |
|---|----------------|
| 1. Frequency Response without a Compensator..... | freq_resp |
| 2. Frequency Response with a Type3 Compensator..... | freq_resp-comp |
| 3. Step-load Transient Response..... | step-load |

Libraries :

1. ..¥boost_sw.lib
2. ..¥erramp.lib

Tool :

- Boost Converter Calculator (Excel sheet)



Boost_Calculator.xls